
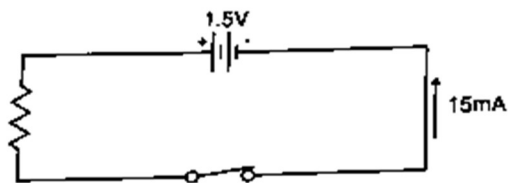



Ohm's Law

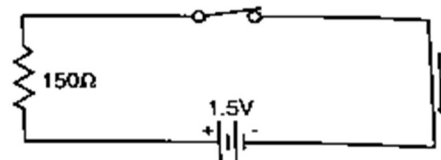


What is the resistance in this circuit? _____



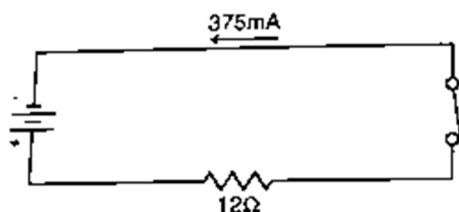
What is the amperage in this circuit? _____



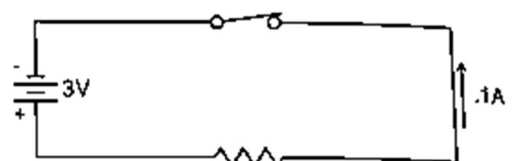What is the voltage in this circuit? _____



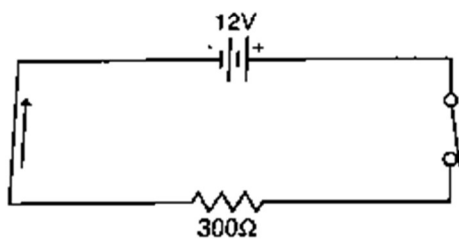What is the resistance in this circuit? _____




What is the amperage in this circuit? _____




What is the resistance in this circuit? _____



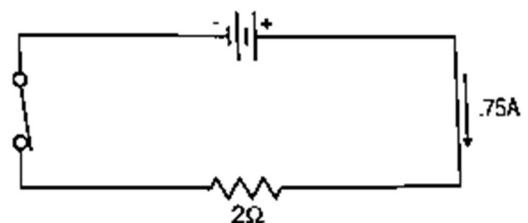
What is the resistance in this circuit? _____



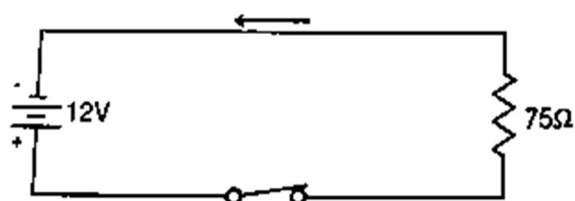
What is the voltage in this circuit? _____



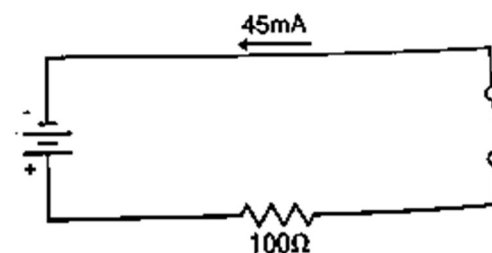
What is the amperage in this circuit? _____



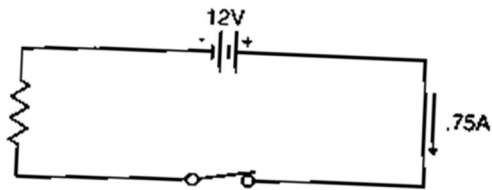What is the voltage in this circuit? _____



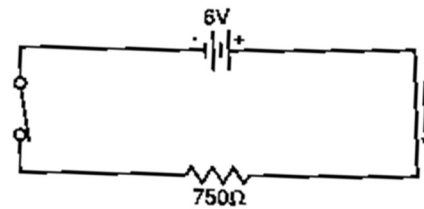
What is the resistance in this circuit? _____




What is the amperage in this circuit? _____



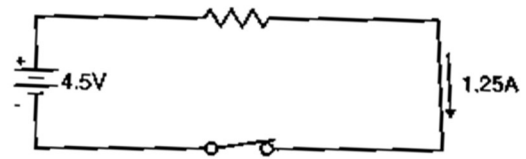
What is the voltage in this circuit? _____



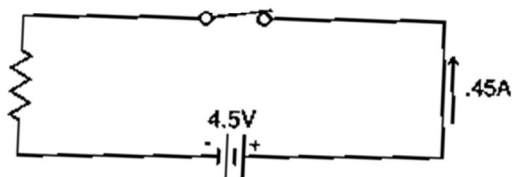
What is the resistance in this circuit? _____



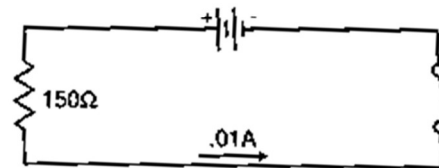
What is the resistance in this circuit? _____



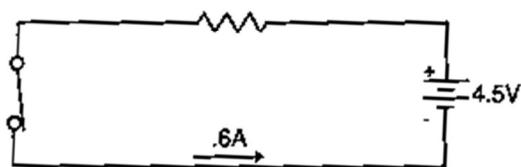
What is the voltage in this circuit? _____



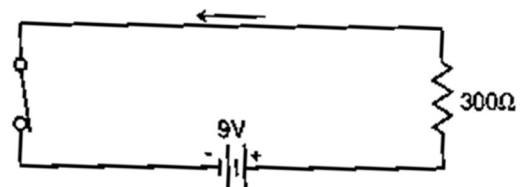
What is the resistance in this circuit? _____



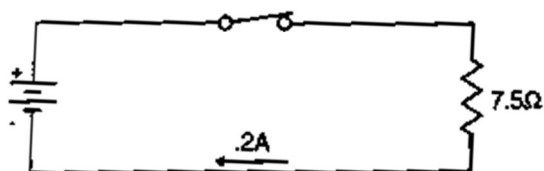
What is the amperage in this circuit? _____



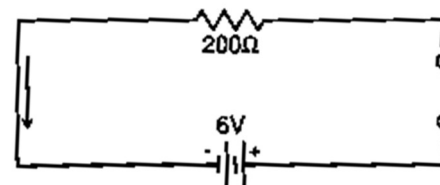
What is the voltage in this circuit? _____



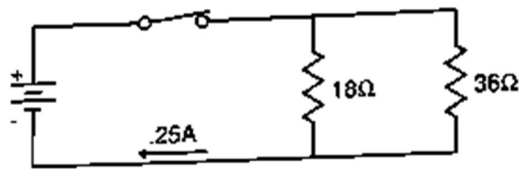
What is the amperage in this circuit? _____



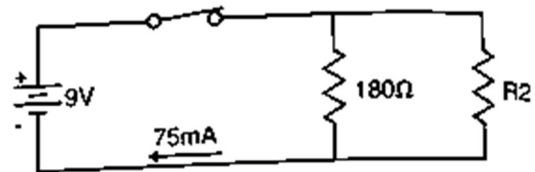
What is the voltage in this circuit? _____




What is the resistance of $R2$? _____

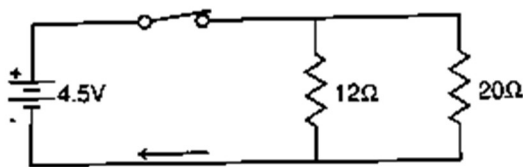

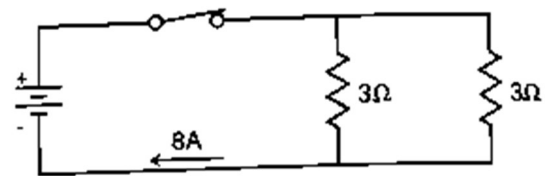
What is the amperage in this circuit? _____



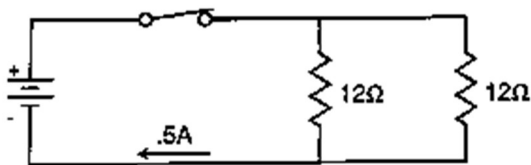
What is the voltage in this circuit? _____



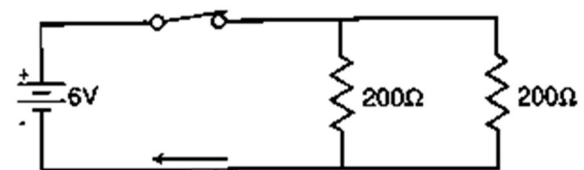
What is the voltage in this circuit? _____



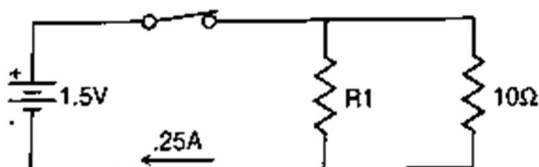
What is the amperage in this circuit? _____




What is the resistance of $R1$? _____

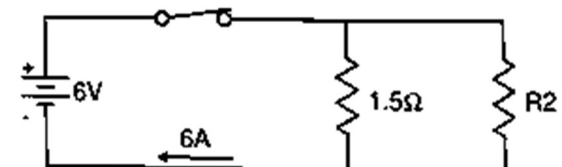


What is the resistance of $R2$? _____

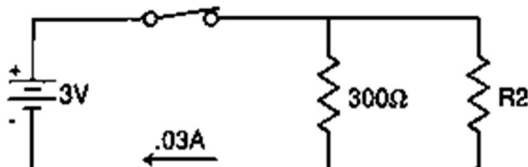


What is the resistance of $R2$? _____

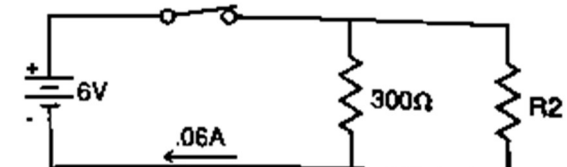


What is the resistance of $R2$? _____

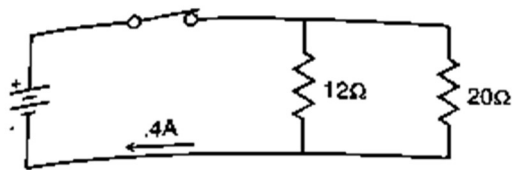

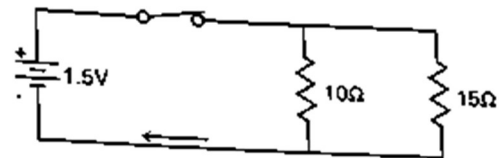
What is the voltage in this circuit? _____



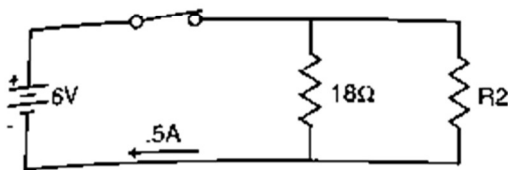
What is the amperage in this circuit? _____




What is the resistance of R2? _____

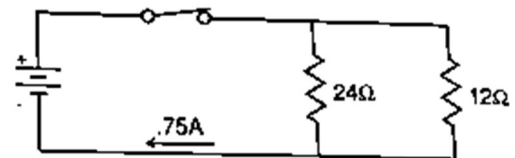

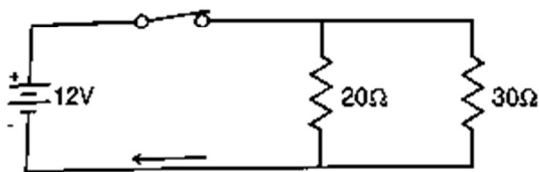
What is the voltage in this circuit? _____



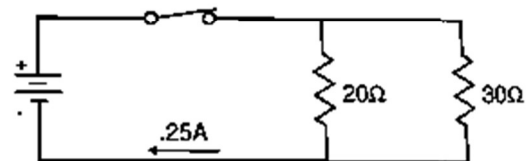
What is the amperage in this circuit? _____



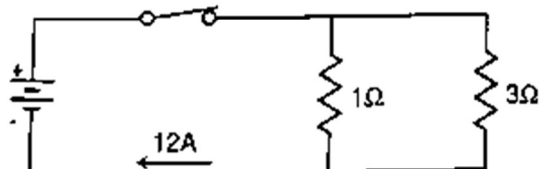
What is the voltage in this circuit? _____



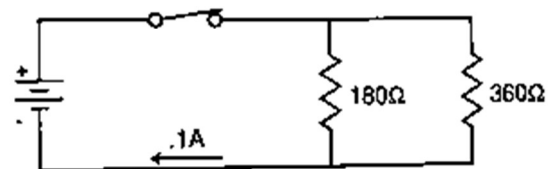
What is the voltage in this circuit? _____



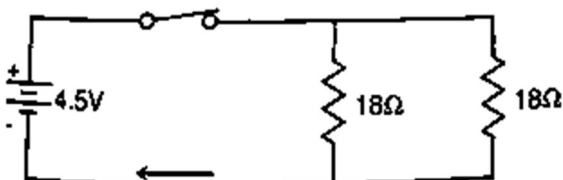What is the voltage in this circuit? _____



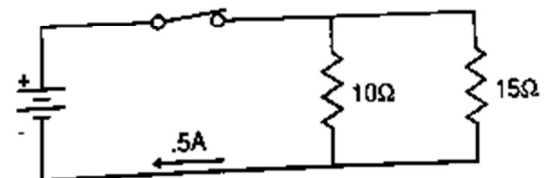What is the amperage in this circuit? _____



What is the voltage in this circuit? _____